

# Architecture des Ordinateurs I

## Part I: VHDL and Logic Design The Language VHDL

[Paolo.Ienne@epfl.ch](mailto:Paolo.Ienne@epfl.ch)

EPFL – I&C – LAP



## Recommended Books:


- ❖ John F. Wakerly  
Digital design (3rd edition)  
Prentice Hall, 2001
- ❖ Peter J. Ashenden  
The designer's guide to VHDL (2nd edition)  
Morgan Kaufmann, 2001
- ❖ Peter J. Ashenden  
The student's guide to VHDL  
Morgan Kaufmann, 1998
- ❖ James R. Armstrong and F. Gail Gray  
VHDL design: Representation and synthesis (2nd edition)  
Prentice Hall, 2000
- ❖ Jacques Weber et Maurice Meaudre  
VHDL: Du langage au circuit, du circuit au langage  
Masson, 1997
- ❖ Roland Airiau, Jean-Michel Bergé, Vincent Olive et Jacques Rouillard  
VHDL: Langage, modélisation, synthèse (2ème édition)  
PPUR, 1998




# Introduction

## A simple traffic-light controller


## Example: A Traffic Light

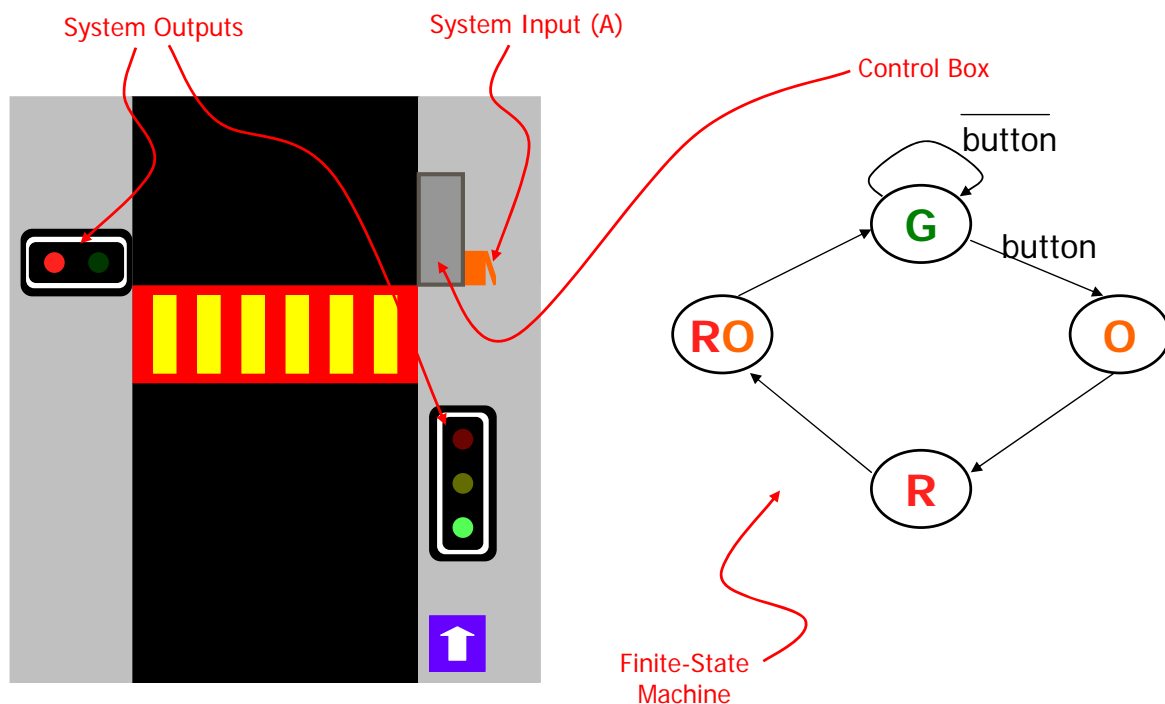


# Control Box

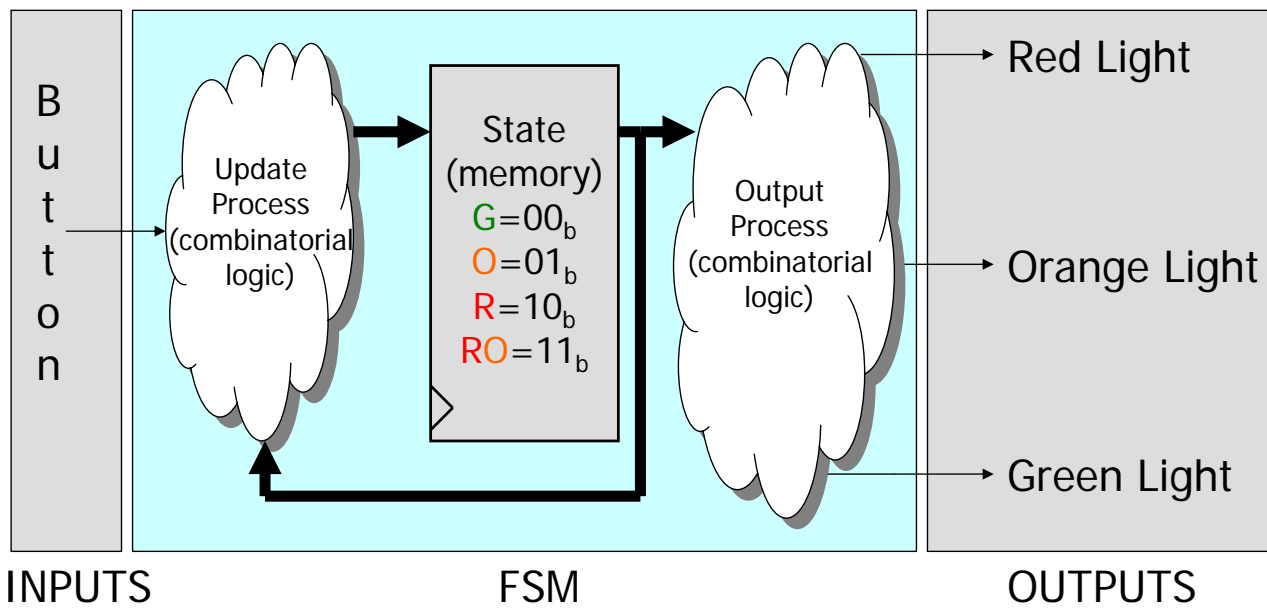


# Classic Approach

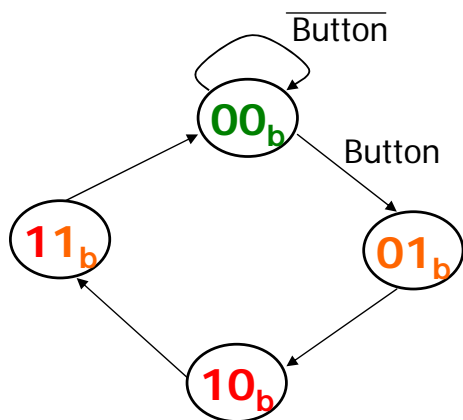



State	B	Next State	Green light	Orange light	Red light
00 <sub>b</sub>	0 <sub>b</sub>	00 <sub>b</sub>	1 <sub>b</sub>	0 <sub>b</sub>	0 <sub>b</sub>
00 <sub>b</sub>	1 <sub>b</sub>	01 <sub>b</sub>	1 <sub>b</sub>	0 <sub>b</sub>	0 <sub>b</sub>
01 <sub>b</sub>	X	10 <sub>b</sub>	0 <sub>b</sub>	1 <sub>b</sub>	0 <sub>b</sub>
10 <sub>b</sub>	X	11 <sub>b</sub>	0 <sub>b</sub>	0 <sub>b</sub>	1 <sub>b</sub>
11 <sub>b</sub>	X	00 <sub>b</sub>	0 <sub>b</sub>	1 <sub>b</sub>	1 <sub>b</sub>

 



# Gate Level Implementation

 

State	B	Next state
00	0	00
00	1	01
01	X	10
10	X	11
11	X	00

  


# Signal Flow

  

# Is This the Way to Go?

- ❑ Design engineers used this method until about 1985
- ❑ For simple designs this method works, but as complexity increases new methodologies are required
- ❑ Compare gate-level designing with writing programs in assembly language
- ❑ We are not going to use gate-level design methods for 1 billion transistors!

## Design Flow

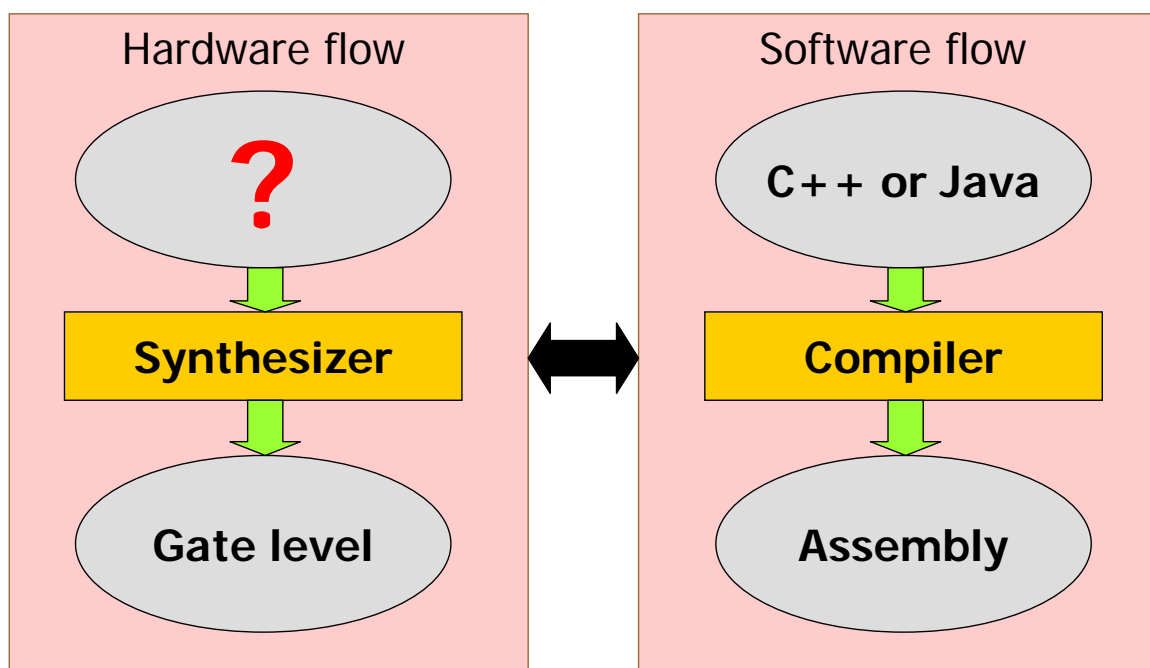

Very High-Speed Integrated Circuits (VHSIC)  
? = VHDL  
Hardware Description Language

- ❑ Formal language for specifying digital systems, equally good at structural as behavioral level
- ❑ Usage:
  - ❖ System description
  - ❖ Simulation
  - ❖ Conceptual modeling
  - ❖ Documentation
- ❑ Main characteristics:
  - ❖ Hierarchical
  - ❖ Event-driven simulation
  - ❖ Modular
  - ❖ Extensible
  - ❖ General language, strongly typed, similar to Ada

## History

- ❑ 1980:  
Beginning of the project, financed by DoD (400M \$US)
- ❑ 1982:  
Contracts for Intermetrics, IBM et Texas
- ❑ 1985:  
Version 7.2 released public domain
- ❑ 1987:  
Standard IEEE 1076 (VHDL-87)
- ❑ 1993:  
New version of the standard (VHDL-93)
- ❑ 2001:  
New version of the standard (VHDL-2001)

## In This Course...

- ❑ VHDL is a very rich language and provides syntactical elements for describing:
  - ❖ Synthesizable digital systems
  - ❖ Functional description of complex components (processors, DSPs, etc.)
  - ❖ Description of libraries of elementary gates with internal delays rise and fall times, etc.
  - ❖ ...
- ❑ We will only use a subset, namely the description of *synthesizable zero-delay digital systems*

## Simulation vs. Synthesis



- ❑ **Simulation:** It is the process of verifying the proper functionality of the VHDL description of a system (similar to **executing** a program in C++ or Java)
- ❑ **Synthesis:** It is the process of translating the VHDL description of a system into simple gates (similar to **compiling** a program in C++ or Java)

# Traffic Light in VHDL

- By using VHDL we can “forget” Boolean algebra, we can describe the functionality
- In our FSM, `next_state` is a function of `state` and `button`

```

  update_process : PROCESS(state,button)
BEGIN
  IF (state = green) THEN
    IF (button = '1') THEN next_state <= orange;
    ELSE next_state <= green;
    END IF;
  ELSIF (state = orange) THEN next_state <= red;
  ELSIF (state = red) THEN next_state <= red_orange;
  ELSE next_state <= green;
  END IF;
END PROCESS update_process;
    
```





# Traffic Light in VHDL

- The outputs are a function of only the current `state` (Moore FSM)

```

  output_process : PROCESS (state)
BEGIN
  IF (state = green) THEN Green_Light <= '1';
  ELSE Green_Light <= '0';
  END IF;
  IF (state = orange OR
      state = red_orange) THEN Orange_Light <= '1';
  ELSE Orange_Light <= '0';
  END IF;
  IF (state = red OR
      state = red_orange) THEN Red_Light <= '1';
  ELSE Red_Light <= '0';
  END IF;
END PROCESS output_process;
    
```






  
# Traffic Light in VHDL

- ❑ And finally, the “memory” of the state has to be modelled
- ❑ Note that the new **state** only depends on **next\_state** and **clk**


```
state_process : PROCESS (clk, next_state)
BEGIN
  IF (clk'event AND clk='1') THEN state <= next_state;
  END IF;
END PROCESS state_process;
```



## Basic Syntactical Rules

- ❑ VHDL is a **case insensitive** language
- ❑ VHDL has a free formatting
- ❑ Each command sequence should be **terminated by a “;”**
- ❑ Remarks can be placed by using **“--” in front of the remark**
- ❑ A remark terminates at the end of the line

# Entity

 

The "black box" is called **ENTITY** in VHDL

The signals going into, or coming from the **ENTITY** are called ports, and are described in the **PORT** section

```
ENTITY fsm IS
  PORT ( B : IN std_logic; -- Button input
        RL : OUT std_logic; -- Red light output
        OL : OUT std_logic; -- Orange light output
        GL : OUT std_logic); -- Green light output
END fsm;
```

# Syntax of the Entity

Each **ENTITY** may have a library definition

We will always use the ones described here  
(similar to `#include <stdlib.h>` in C/C++)

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;

ENTITY <entity_name> IS
  PORT ( ... );
END <entity_name>;
```

Each **ENTITY** may have a port section

Each **ENTITY** requires a unique name

# Syntax of the Port Section

Each **PORT** requires a unique name

Each **PORT** requires a signal type

```
PORT ( <port_name> : <port_type> <signal_type>;  
      <port_name> : <port_type> <signal_type>;  
      .  
      <port_name> : <port_type> <signal_type>;  
      <port_name> : <port_type> <signal_type>;  
);
```

### IMPORTANT NOTE:

The last port in the **PORT** section is not terminated by a ;

Each **PORT** requires a type, which can be:

**IN** => The port is an input port (Read Only)

**OUT** => The port is an output port (Write Only)

**INOUT** => The port is bidirectional (Read and Write)

We will seldom (maybe never...) use **INOUT** ports

# (Signal) Types in VHDL

□ VHDL knows various types, like:

- ❖ Real
- ❖ Integer
- ❖ Time
- ❖ ...

We will seldom (or never...) use standard types

□ In this course we are only going to use the following VHDL types:

- ❖ **STD\_LOGIC** → This is the type holds a one bit quantity (see it as being one wire)
- ❖ **STD\_LOGIC\_VECTOR ((n-1) DOWNTO 0)** → This type holds a set of n-bits (see it as being a collection of n wires)

□ Furthermore we are going to use own defined types, which can come in handy in FSMs (as we will later see):

- ❖ **TYPE state\_type IS (Green, Orange, Red, RedOrange)**
- ❖ **TYPE hex\_type IS (1,2,3,4,5,6,7,8,9,A,B,C,D,E,F)**

# STD\_LOGIC and STD\_LOGIC\_VECTOR

- The **STD\_LOGIC** and each element (“bit”) of the **STD\_LOGIC\_VECTOR** can hold nine values:
  - ❖ 'U' = uninitialized
  - ❖ 'X' = forcing unknown
  - ❖ '0' = forcing 0
  - ❖ '1' = forcing 1
  - ❖ 'Z' = high impedance
  - ❖ 'W' = weak unknown
  - ❖ 'L' = weak 0 (pull-down)
  - ❖ 'H' = weak 1 (pull-up)
  - ❖ '-' = don't care
- In this course we will **ONLY** use and consider the values 'U', 'X', '0', '1' and 'Z' !

## Our Entity

We of course need also a clock input  
for our memory elements

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;

ENTITY fsm IS
  PORT ( CLK           : IN  std_logic;  -- Clock input
        Button        : IN  std_logic;
        Red_Light     : OUT std_logic;
        Orange_Light  : OUT std_logic;
        Green_Light   : OUT std_logic);
END fsm;
```

**BUT: Where is the functionality of this black-box?**

# Functionality

```
ARCHITECTURE functional_level OF fsm IS
```

```
TYPE fsm_state_t IS (green,orange,red,red_orange);
SIGNAL state      : fsm_state_t;
SIGNAL next_state : fsm_state_t;
```

```
BEGIN
```

```
update_process : PROCESS(state,button)
BEGIN
```

```
IF (state = green) THEN
  IF (button = '1') THEN next_state <= orange;
  ELSE next_state <= green;
END IF;
ELSIF (state = orange) THEN next_state <= red;
ELSIF (state = red) THEN next_state <= red_orange;
ELSE next_state <= green;
END IF;
```

```
END PROCESS update_process;
```

```
output_process : PROCESS (state)
```

```
BEGIN
```

```
IF (state = green) THEN Green_Light <= '1';
ELSE Green_Light <= '0';
END IF;
IF (state = orange OR
state = red_orange) THEN Orange_Light <= '1';
ELSE Orange_Light <= '0';
END IF;
IF (state = red OR
state = red_orange) THEN Red_Light <= '1';
ELSE Red_Light <= '0';
END IF;
```

```
END PROCESS output_process;
```


```
state_process : PROCESS (clk, next_state)
```

```
BEGIN
```


```
IF (clk'event AND clk='1') THEN state <= next_state;
END IF;
```

```
END PROCESS state_process;
```

```
END functional_level;
```

 

# Architecture

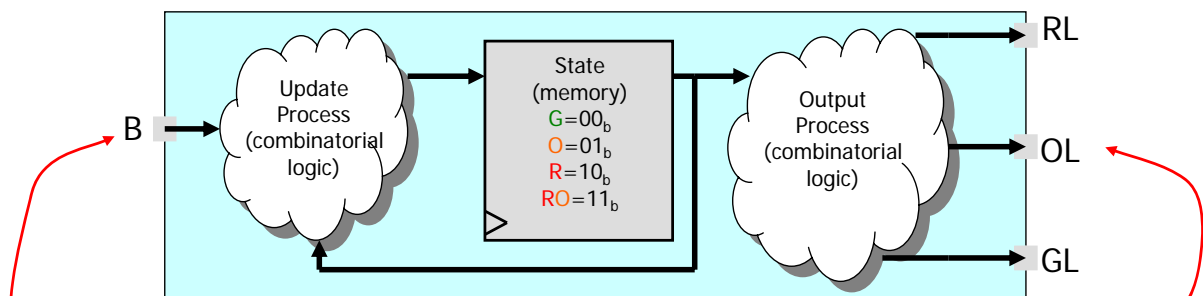

The functionality of the black box is described in VHDL in the **ARCHITECTURE** section

The ports are defined in the **PORT** section of the **ENTITY** declaration, and are therefore **inherently known** in the **ARCHITECTURE**

```
ARCHITECTURE implementation_1 OF fsm IS
```


```
...
```

```
BEGIN
```

```
...
```

```
END implementation_1;
```

# Architecture and Entity Relationship

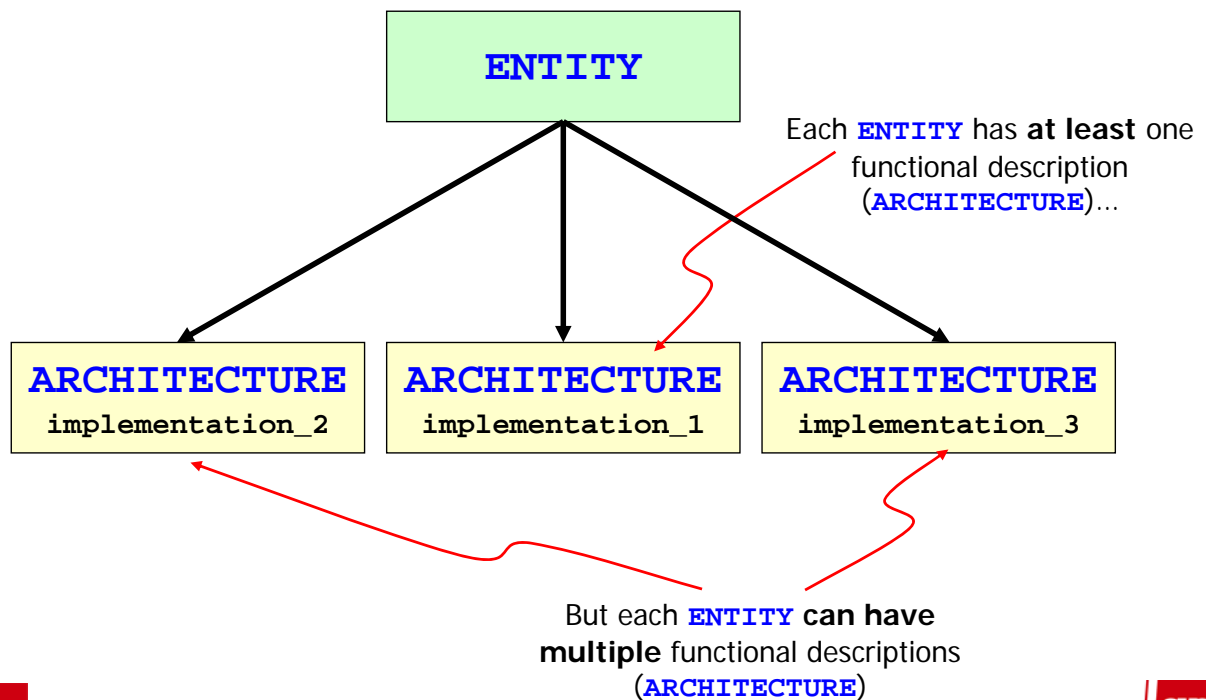

## Syntax of the Architecture

Each **ARCHITECTURE** definition can contain declarations (Similar: `int loop;` in C++)

Each **ARCHITECTURE** section is **referenced** to its corresponding **ENTITY** definition **by the name** of this **ENTITY**

```
ARCHITECTURE <implementation_name> OF <entity_name> IS
  [Declaration Section]
BEGIN
  [Body]
END <implementation_name>;
```

The body of the **ARCHITECTURE** contains the actual functionality


Each **ARCHITECTURE** section has its own unique implementation name

# Declaration Section

- ❑ The declaration section of an **ARCHITECTURE** can contain:
  - ❖ **SIGNAL** declarations. Signals are the “wires” or “state” of the circuit.
  - ❖ **CONSTANT** definitions. Constants are fixed value “wires” or fixed value “state” within the circuit.
  - ❖ **COMPONENT** declarations. Components give us the possibility to design hierarchical.
  - ❖ **FUNCTION** definitions. Functions can be used for actions which are often required in the functional description
  - ❖ **PROCEDURE** definitions. Similar to Functions also procedures can be used.
- ❑ In this course we will only use the **signal**, **constant**, and eventually the **component**.
- ❑ Each of this topics will be defined later on in this course.

 
# Body of an Architecture

- ❑ The body of an architecture consists of:
  - ❖ Implicit processes
  - ❖ Explicit processes
  - ❖ Component instantiations
- ❑ Each of these topics will be used in this course and will be introduced later on
- ❑ Each of these parts execute in parallel (in contrast with software programming languages where instructions are executed sequentially!)


 
# Creation of the Body Structure

- ❑ Most VHDL code written and used nowadays by designers is written following the **RTL (=Register Transfer Level)** principle. In this course we will only design using this principle.
- ❑ The RTL principle consists of separating the sequential processes (e.g., memory, flip-flops and latches) from the combinatorial processes. Finally we connect the different processes by wires.
- ❑ How do we do this:
  - ❖ Identify the combinatorial and sequential elements.
  - ❖ Write the VHDL code for all these elements.
  - ❖ Control that no memory action is introduced in the combinatorial elements (to be elaborated later on in this course).
  - ❖ Connect the elements by using wires (e.g., signals).



# Summary

```


LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;

ENTITY <entity_name> IS
  PORT ( <port_name> : <port_type> <signal_type>;
        <port_name> : <port_type> <signal_type>;
        .
        <port_name> : <port_type> <signal_type>;
        <port_name> : <port_type> <signal_type>
        );
END <entity_name>;

ARCHITECTURE <implementation_name> OF <entity_name> IS

  [Declaration Section]

 BEGIN
  [Body]
END <implementation_name>;
    
```






# 2

## The body of an ARCHITECTURE

Signals as wires  
Operators  
Statements  
Events  
Implicit processes
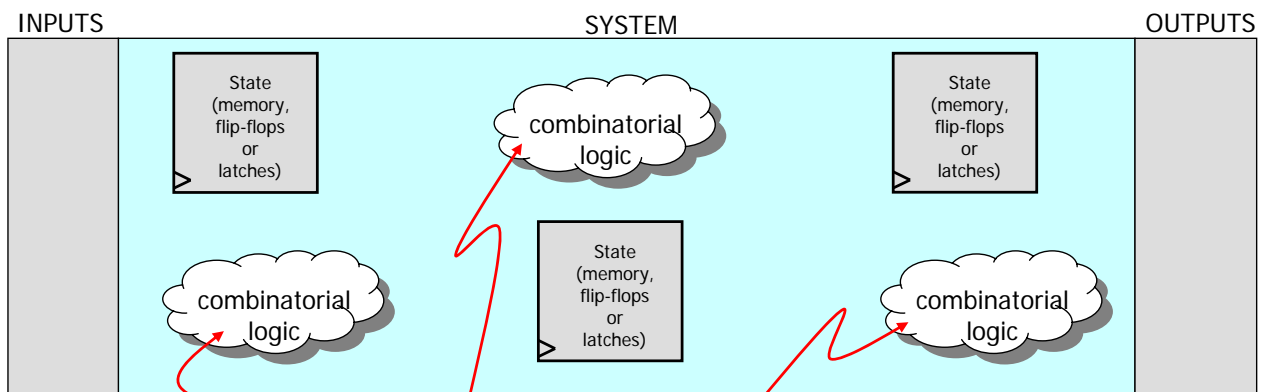
## Remember RTL


- We will divide each system (**ARCHITECTURE**) into:
  - ❖ Combinatorial elements
  - ❖ Elementary sequential elements (memory, flip-flop and/or latches)
  - ❖ Interconnects (wires)
- Each combinatorial and sequential element form a **PROCESS** inside the **ARCHITECTURE** and all execute in parallel



In this lecture we will concentrate on the combinatorial elements
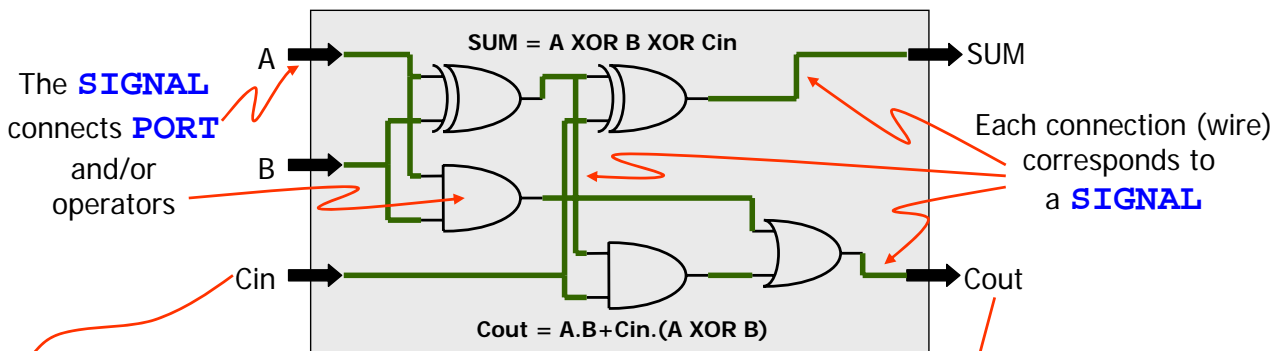
# Combinatorial Element: The Full Adder

- The Full Adder is a typical example of combinatorial logic



- Remember how the **entity** is defined:

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;

ENTITY full_adder IS
  PORT ( A      : IN  std_logic; -- A input
        B      : IN  std_logic; -- B input
        Cin    : IN  std_logic; -- Carry input
        SUM    : OUT std_logic; -- Sum output
        Cout   : OUT std_logic); -- Carry output
END full_adder;
    
```

# Signal Syntax

Each **SIGNAL** has its own unique name

Each **SIGNAL** has a signal type (see the previous lecture on these types)

```
SIGNAL <signal_name>[, <signal_name>,...] : <signal_type>;
```

And all **SIGNAL**'s are defined in the declaration section of the **ARCHITECTURE**

It is good practice, but not required, to prefix all signal names with "s\_"


```

ARCHITECTURE <implementation_name> OF <entity_name> IS
  [Declaration Section]
BEGIN
  [Body]
END <implementation_name>;
    
```



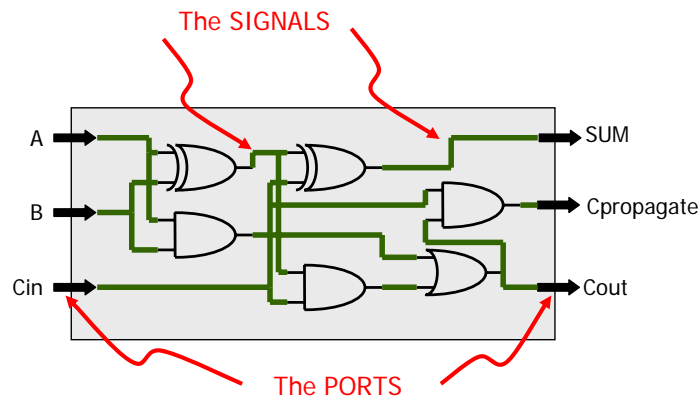
# Signals and Ports

- ❑ Each connection that is used in the body of the **ARCHITECTURE**, is called a **SIGNAL**
- ❑ **PORT**'s are defined in the **ENTITY** and can be used in the body of the **ARCHITECTURE**
- ❑ **PORT**'s have a slightly odd behavior:
  - ❖ Input **PORT**'s can **only** be **read**, but they **cannot** be **assigned** a value
  - ❖ Output **PORT**'s can **only** be **assigned** a value, but they **cannot** be **read**



# Ports: A Typical Mistake

 

```
SUM    <= A XOR B XOR Cin;
Cout   <= (A AND B) OR (Cin AND (A XOR B));
Cpropagate <= Cin AND Cout;
```

**NO**

As Cout is an output port, it cannot be read! Hence this is not a correct implementation

```
SUM <= A XOR B XOR Cin;
s_x8 <= (A AND B) OR (Cin AND (A XOR B));
Cout <= s_x8;
Cpropagate <= s_x8 AND Cin;
```

We have to introduce an explicit signal s\_x8, to make a correct implementation

# Different Implementations

Extensive signal usage:

```

s_x1 <= A;
s_x2 <= B;
s_x3 <= Cin;
s_x4 <= s_x1 XOR s_x2;
s_x5 <= s_x4 XOR s_x3;
SUM <= s_x5;

s_x6 <= s_x1 AND s_x2;
s_x7 <= s_x3 AND s_x4;
s_x8 <= s_x6 OR s_x7;
Cout <= s_x8;

s_x9 <= s_x8 AND s_x3;
Cpropagate <= s_x9;
    
```


"Merging" of signals:

```

SUM <= A XOR B XOR Cin;

s_x8 <= (A AND B) OR (Cin AND (A XOR B));
Cout <= s_x8;

Cpropagate <= s_x8 AND Cin;
    
```

 

s\_x8 must stay, as it has the output PORT cannot be read!

# Operators

❑ To model the functionality of the system, VHDL provides several operators:

- ❖ Logical:
  - and or nand nor xor xnor not
- ❖ Comparison:
  - = /= < <= > >=
- ❖ Concatenation:
  - &
- ❖ Arithmetic:
  - + - \* / mod rem
- ❖ Shifting:
  - sll srl sla sra rol ror
- ❖ Sign:
  - + -
- ❖ Diverse:
  - abs \*\*

← These operators we will use

← We will only use + and - of this set of operators

← These operators "make no sense" in std\_logic and std\_logic\_vector types, as we can use the concatenation

← These operators we will not use

# Sizes and Concatenation

- ❑ An operator can only work on signals of the same size

```
SIGNAL s_x1 : std_logic_vector(3 DOWNTO 0);
SIGNAL s_x2 : std_logic_vector(3 DOWNTO 0);
SIGNAL s_x3 : std_logic_vector(3 DOWNTO 0);
SIGNAL s_x4 : std_logic_vector(3 DOWNTO 0);
SIGNAL s_x5 : std_logic_vector(1 DOWNTO 0);
SIGNAL s_x6 : std_logic;

s_x3 <= s_x1 XOR s_x2; --This is correct as s_x1,s_x2 and s_x3 all contain 4 bits (wires)
s_x4 <= s_x1 OR s_x5; --This is incorrect as s_x5 only contains 2 bits, whilst s_x1 and s_x4 contain 4
s_x6 <= s_x3 OR s_x4; --This is incorrect as the result of s_x3 OR s_x4 is 4 bits, each operator does
--a bitwise operation (similar to | in C++; || does not exist in VHDL)
```

- ❑ We can increase the size of a signal by using the concatenation operator `&`, or the wire selection operation `( )`

```
SIGNAL s_x1 : std_logic_vector(3 DOWNTO 0);
SIGNAL s_x2 : std_logic_vector(3 DOWNTO 0);
SIGNAL s_x3 : std_logic_vector(3 DOWNTO 0);
SIGNAL s_x4 : std_logic_vector(3 DOWNTO 0);
SIGNAL s_x5 : std_logic_vector(1 DOWNTO 0);
SIGNAL s_x6 : std_logic;

s_x3 <= s_x1 XOR s_x2; --This is correct as s_x1, s_x2 and s_x3 all contain 4 bits (wires)
s_x4 <= s_x1 OR ("00" & s_x5); --This is correct as ("00" & s_x5), s_x1 and s_x4 all contain 4 bits
s_x6 <= s_x3(0) OR s_x4(2); --This is correct as s_x6, s_x3(0) and s_x4(2) all contain 1 bit
```

# Signed and Unsigned

- ❑ The types `std_logic` and `std_logic_vector` can hold signed, but also unsigned values, the synthesizer has no information on this
- ❑ To make clear to the synthesizer what implementation we want when we use arithmetic operators, we can use the type cast `signed(<signal_name>)` or `unsigned(<signal_name>)` in the `<source>` section (we cannot mix them!)
- ❑ Examples

```
Correct:
s_signed_add      <= signed( s_in1 )  + signed( s_in2 );
s_unsigned_add   <= unsigned( s_in3 ) + unsigned( s_in4 );
s_signed_multiply <= signed( s_in1 )  * signed( s_in2 );
s_unsigned_multiply <= unsigned( s_in3 ) * unsigned( s_in4 );
```

```
NOT TO BE USED:
s_mixed_add      <= signed( s_in1 )  + unsigned( s_in3 );
s_mixed_multiply <= signed( s_in1 )  * unsigned( s_in3 );
```

# Special Operations

- We can perform shifting by using concatenation

```
SIGNAL s_x1 : std_logic_vector( 3 DOWNTO 0 );
SIGNAL s_x2 : std_logic_vector( 3 DOWNTO 0 );
SIGNAL s_x3 : std_logic_vector( 3 DOWNTO 0 );

s_x1 <= s_x2( 2 DOWNTO 0 ) & "0";      -- s_x1 is s_x2 << 1; hence s_x1 = s_x2*2...
s_x3 <= s_x2(3) & s_x2( 3 DOWNTO 1 ); -- s_x3 is signed(s_x2) >> 1; hence s_x3 = s_x2/2...
```

- We can use concatenation to extract the carry out

```
SIGNAL s_a : std_logic;
SIGNAL s_b : std_logic;
SIGNAL s_add : std_logic_vector( 1 DOWNTO 0 );
SIGNAL s_sum : std_logic;
SIGNAL s_cout: std_logic;

s_add <= unsigned("0" & s_a) + unsigned("0" & s_b);
s_sum <= s_add(0);
s_cout <= s_add(1);
```

- Important note:

- ❖ For the operators + and -, the synthesizer does not know if a `std_logic_vector` is in a signed, or an unsigned representation
- ❖ We use the typecasts `unsigned(<std_logic_vector>)` and `signed(<std_logic_vector>)` to tell the synthesizer the representation

# Back to the Full Adder

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;

ENTITY full_adder IS
    PORT ( A : IN std_logic; -- A input
          B : IN std_logic; -- B input
          Cin : IN std_logic; -- Carry input
          SUM : OUT std_logic; -- Sum output
          Cprop: OUT std_logic; -- Carry propagate
          Cout : OUT std_logic); -- Carry output
END full_adder;

ARCHITECTURE implementation_1 OF full_adder IS

    SIGNAL s_x8 : std_logic;

BEGIN
    SUM <= A XOR B XOR Cin;
    s_x8 <= (A AND B) OR (Cin AND (A XOR B));
    Cout <= s_x8;
    Cprop <= s_x8 AND Cin;
END implementation_1;
```

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;

ENTITY full_adder IS
    PORT ( A : IN std_logic; -- A input
          B : IN std_logic; -- B input
          Cin : IN std_logic; -- Carry input
          SUM : OUT std_logic; -- Sum output
          Cprop: OUT std_logic; -- Carry propagate
          Cout : OUT std_logic); -- Carry output
END full_adder;

ARCHITECTURE implementation_1 OF full_adder IS

    SIGNAL s_x8 : std_logic;

BEGIN
    Cprop <= s_x8 AND Cin;
    SUM <= A XOR B XOR Cin;
    Cout <= s_x8;
    s_x8 <= (A AND B) OR (Cin AND (A XOR B));
END implementation_1;
```

?

=

Remember that by definition:  
All elements in the body of an  
**ARCHITECTURE** are either  
**PROCESS**'s or **COMPONENT**'s.  
This architecture thus contains 4  
(implicit) **PROCESS**'es

**YES, both full\_adder's are equal!**  
As all **PROCESS**'es and **COMPONENT**'s execute  
in parallel, their order does not matter!  
**Note: For Java and C++ this is different,**  
**as they execute all lines sequentially!**

# Back to the Full Adder

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;


ENTITY full_adder IS
  PORT ( A : IN std_logic; -- A input
        B : IN std_logic; -- B input
        Cin : IN std_logic; -- Carry input
        SUM : OUT std_logic; -- Sum output
        Cprop : OUT std_logic; -- Carry propagate
        Cout : OUT std_logic); -- Carry output
END full_adder;

ARCHITECTURE implementation_1 OF full_adder IS

  SIGNAL s_x8 : std_logic;

BEGIN
  SUM <= A XOR B XOR Cin;
  s_x8 <= (A AND B) OR (Cin AND (A XOR B));
  Cout <= s_x8;
  Cprop <= s_x8 AND Cin;
END implementation_1;

```

 


Intuition:  
All elements in hardware will execute in parallel, hence the processes must also execute in parallel

# Sensitivity and Trigger

- A process is said to be *sensitive* to a wire, if and only if the output of the process can change in case the wire changes its value

Process 1 is sensitive to A,B and Cin

 

Process 5 is sensitive to s\_x8, but also to s\_x9!

Process 3 is sensitive to s\_x8

Process 2 is sensitive to A,B and Cin


Process 4 is sensitive to s\_x8 and Cin

- A process is triggered if one or more wires, to which the process is sensitive, change its/their value



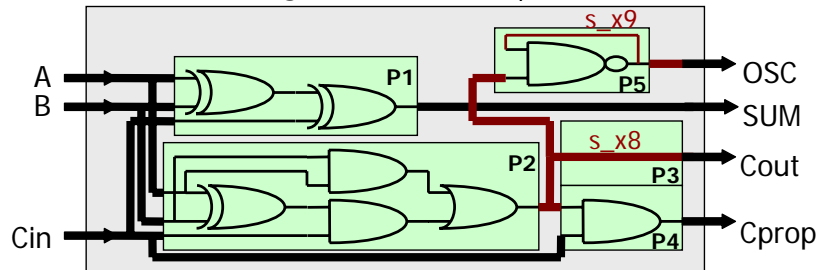
# Delta

- Assume that every **PROCESS** has an input to output delay of  $\delta$
- If A, B, and/or Cin change(s) at time  $t_1$ , this is how simulation goes



 Note:  
 $\delta$  does not include the gate delays, as we are working with a zero delay model!



# Delta

- We assumed the input and output delay to be  $\delta$ , but in reality  $\delta \rightarrow 0$
- Delta is defined as the number of  $\delta$  steps we need to take until all **PROCESS**'es produce a stable output (no process is triggered):
  - PROCESS** 1 and 2 produce a stable output after Delta = 1
  - PROCESS** 3 and 4 produce a stable output after Delta = 2
  - PROCESS** 5 does not produce a stable output, as it is triggered over and over again
- An **ARCHITECTURE** which does not produce a stable output on all its **PROCESS**'es, after a finite number of  $\delta$  steps, is called instable, and cannot be simulated.
- We will only use stable **ARCHITECTURE**'s, hence Delta is finite

Notes:

- We can of course model oscillators (instable architectures), by also modeling the gate delay, but this is outside the scope of this course
- Instable architectures can be implemented in hardware, and are thus synthesizable

# Processes and Components

- Each "element" or "box" in our **ARCHITECTURE BODY** is a process:

```
<process_name> : PROCESS ([Sensitivity List])  
  
    [Declaration Section]  
  
BEGIN  
    [Process description]  
END PROCESS <process_name>;
```

Explicit form

Implicit form

```
<signal_name> <= <source>;
```

- Or a component:

```
<component_reference> : <component_name>  
    GENERIC MAP ( [generic mappings] )  
    PORT MAP ( [Port connections] );
```

## Implicit Processes

- We have seen **PROCESS**'es in the form:

```
<signal_name> <= <source>;
```

- This are so called **implicit PROCESS**'s
- Implicit **PROCESS**'es are by definition sensitive to all **SIGNAL**'s listed in the **<source>**, and thus are triggered by a change on these signals
- Implicit **PROCESS**'es are not embedded into a **PROCESS** container
- In implicit **PROCESS**'es the **<source>** consists of signals and operators
- There exists a special implicit **PROCESS**, the **WHEN ... ELSE ...;** construct

# Implicit Constructs

## □ Syntax:

The **ELSE** part must always be present, as otherwise the **SIGNAL** is not always assigned a value!

```
<signal_name> <= <source1> WHEN <condition> ELSE  
    <source2>;  
<signal_name> <= <source1> WHEN <condition1> ELSE  
    <source2> WHEN <condition2> ELSE  
    ...  
    <sourceN>;
```


## □ Example:

**Question:**

What is the hardware representing this construct?

```
next_state <= green WHEN state = red_orange OR  
    (state = green AND  
    button /= '1') ELSE  
    orange WHEN state = green AND  
    button = '1' ELSE  
    red WHEN state = orange ELSE  
    red_orange;
```

**Answer:**

 

# Summary

- The **SIGNAL**'s in the body of an **ARCHITECTURE** represent the wires of the system connecting the **PORT**'s and the operators
- The operators define the functionality of the system
- **SIGNAL**'s may only be assigned once
- Each element in the body of an **ARCHITECTURE** is a **PROCESS** or a **COMPONENT**
- **PROCESS**'es and **COMPONENT**'s execute in parallel

# 3

## Sequential Logic

Explicit processes  
Latches  
Flip-flops and Registers  
Components

## Reminder Processes and Components

- Each "element" or "box" in our **ARCHITECTURE BODY** is a process:

```
<process_name> : PROCESS ([Sensitivity List])  
  
    [Declaration Section]  
  
    BEGIN  
        [Process description]  
    END PROCESS <process_name>;
```

Explicit form

Implicit form

```
<signal_name> <= <source>;
```

- Or a component:

```
<component_reference> : <component_name>  
    GENERIC MAP ( [generic mappings] )  
    PORT MAP ( [Port connections] );
```

# Explicit Process

- ❑ A **PROCESS** which is not implicit is called an **explicit PROCESS**
- ❑ An explicit **PROCESS** can be converted to one or multiple implicit one(s) if and only if it contains **only** combinatorial logic
- ❑ An explicit **PROCESS** is **not** inherently sensible to its inputs
- ❑ The body of an explicit **PROCESS** executes **in program order**

# Explicit Process Syntax

Each **PROCESS** has a  
unique name

Each **PROCESS** can have  
a sensitivity list

```
<process_name> : PROCESS ([Sensitivity List])  
  
    [Declaration Section]  
  
    BEGIN  
    → [Process body]  
    END PROCESS <process_name>;
```

Each **PROCESS** has  
a body

Each **PROCESS** can have  
a declaration section

Note:

We can also just write **END PROCESS;**

# Sensitivity List

- ❑ Explicit **PROCESS**'s are not inherently sensitive to their inputs, to make the **PROCESS** sensitive to (and thus trigger on a change of) a **SIGNAL**, the name of this **SIGNAL** can be put in the sensitivity list:

```
example_process : PROCESS ( <signal_name>, ... , <signal_name> )
```

- ❑ Example, a two input NAND gate:

```
SIGNAL s_a : std_logic;  
SIGNAL s_b : std_logic;  
SIGNAL s_q : std_logic;
```

We will **ALWAYS** put **all signals** which appear after **all** assignment commands (`<=` and `:=`) in the **sensitivity list** of an explicit process

```
Nand_gate1 : PROCESS ( s_a , s_b )  
BEGIN  
    s_q <= s_a NAND s_b;  
END PROCESS nand_gate1;
```

?

=

```
Nand_gate2 : PROCESS ( s_a )  
BEGIN  
    s_q <= s_a NAND s_b;  
END PROCESS nand_gate2;
```

In hardware both are equal, but **NOT** in simulation!

**nand\_gate2** will **only** be triggered by a change on **s\_a**, and **not** by a change on **s\_b**!

The synthesizer will issue a **warning** when it encounters such a construct

# Declaration Section

- ❑ The declaration section of an explicit **PROCESS** can contain **VARIABLE** instantiations
- ❑ The declaration section of an explicit **PROCESS** can contain **SIGNAL** instantiations, which are local to this **PROCESS**
- ❑ The declaration section of an explicit **PROCESS** can contain **CONSTANT** instantiations, which are local to this **PROCESS**

# Variables

- ❑ **VARIABLE**'s have a similar syntax as **SIGNAL**'s

```
VARIABLE <variable_name>[, <variable_name>,...] : <signal_type>;
```

It is good practice, but not required,  
to prefix all variable names with "v\_"

- ❑ **VARIABLE**'s can **only** exist inside an explicit **PROCESS**,  
and are local to this **PROCESS**

- ❑ **VARIABLE**'s can be assigned a value by using

```
<variable_name> := <source>;
```

**Note:**  
We need := and not <=

## Back to the Full Adder

Using implicit **PROCESS**'es:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;

ENTITY full_adder IS
  PORT ( A      : IN  std_logic; -- A input
         B      : IN  std_logic; -- B input
         Cin    : IN  std_logic; -- Carry input
         SUM    : OUT std_logic; -- Sum output
         Cprop  : OUT std_logic; -- Carry propagate
         Cout   : OUT std_logic); -- Carry output
END full_adder;

ARCHITECTURE implementation_1 OF full_adder IS

  SIGNAL s_x8 : std_logic;

BEGIN
  SUM  <= A XOR B XOR Cin;
  s_x8 <= (A AND B) OR (Cin AND (A XOR B));
  Cout <= s_x8;
  Cprop <= s_x8 AND Cin;
END implementation_1;
```

=

Using one explicit **PROCESS**:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;

ENTITY full_adder IS
  PORT ( A      : IN  std_logic; -- A input
         B      : IN  std_logic; -- B input
         Cin    : IN  std_logic; -- Carry input
         SUM    : OUT std_logic; -- Sum output
         Cprop  : OUT std_logic; -- Carry propagate
         Cout   : OUT std_logic); -- Carry output
END full_adder;

ARCHITECTURE implementation_2 OF full_adder IS

BEGIN
  adder : PROCESS( A , B , Cin )
    VARIABLE v_x8 : std_logic;
  BEGIN
    SUM  <= A XOR B XOR Cin;
    v_x8 := (A AND B) OR (Cin AND (A XOR B));
    Cout <= v_x8;
    Cprop <= v_x8 AND Cin;
  END PROCESS adder;
END implementation_2;
```

# Back to the Full Adder

With implicit **PROCESS**'s, we have seen that:

<pre>BEGIN SUM  &lt;= A XOR B XOR Cin; s_x8 &lt;= (A AND B) OR (Cin AND (A XOR B)); Cout &lt;= s_x8; Cprop &lt;= s_x8 AND Cin; END implementation_1;</pre>	=	<pre>BEGIN Cprop &lt;= s_x8 AND Cin; SUM  &lt;= A XOR B XOR Cin; Cout &lt;= s_x8; s_x8 &lt;= (A AND B) OR (Cin AND (A XOR B)); END implementation_1;</pre>
--	---	--

What about the explicit **PROCESS**'s:

<pre>BEGIN   adder : PROCESS( A , B , Cin )     VARIABLE v_x8 : std_logic;   BEGIN     SUM  &lt;= A XOR B XOR Cin;     v_x8 := (A AND B) OR (Cin AND (A XOR B));     Cout &lt;= v_x8;     Cprop &lt;= v_x8 AND Cin;   END PROCESS adder; END implementation_2;</pre>	≠	<pre>BEGIN   adder : PROCESS( A , B , Cin )     VARIABLE v_x8 : std_logic;   BEGIN     Cprop &lt;= v_x8 AND Cin;     SUM  &lt;= A XOR B XOR Cin;     Cout &lt;= v_x8;     v_x8 := (A AND B) OR (Cin AND (A XOR B));   END PROCESS adder; END implementation_2;</pre>
--	---	--

These two implementations are **not** equal!

Due to the fact that these are now **inside** the body of the process, they are not any longer **separate processes**, but **statements**. And statements execute **in program order** inside the body of an explicit process, and **not in parallel!** We will go into more detail

# Statements and Signals

- Note that the **<=** has a different meaning in an implicit **PROCESS**, and when used in a statement
  - ❖ Using **<=** in an implicit process means **assign immediately**
  - ❖ Using **<=** in a statement means **schedule an assignment**
- The explicit process has some "strange" behavior when it comes to signals

<pre>example : PROCESS( A , B , C ) BEGIN   C &lt;= A OR B;   IF (A AND B) = '1' THEN     C &lt;= '0';   END IF;   X2 &lt;= C; END PROCESS example;</pre>	<p>The process "fixes" the values of the signals when it is triggered</p> <p>The statements within the process <b>schedule</b> new assignments to a signal</p> <p>The process assigns the new values of the signals when it is finished</p> <p>Hence, X2 is assigned the <b>old</b> value of C</p>
---	--

- Note further that **x2** and **c** are only **assigned once** a value, namely **at the end of the PROCESS**



# Statements and Variables

- It's getting even more "strange", as **VARIABLE**'s are assigned immediately in explicit **PROCESS**'es, hence **:=** means **assign immediately**
- Thus

**IMPORTANT:**  
**:=** can **ONLY** be used with variables!

```
example : PROCESS( A , B , C )
  VARIABLE v_x : std_logic;
BEGIN
  v_x := A OR B;
  IF (A AND B) = '1' THEN
    v_x := '0';
  END IF;
  X2 <= v_x;
  c <= v_x;
END PROCESS example;
```

The difference with Signals and Variables, is that **v\_x** is now **assigned** immediately a value, and not just **scheduled** a new assignment!

## Explicit Constructs

- Similar to the **WHEN ... ELSE ...;** construct, we have the **IF ... END IF;** construct in an explicit process:

```
IF <condition> THEN [Statement(s)];
END IF;

IF <condition> THEN [Statement(s)];
  ELSE [Statement(s)];
END IF;

IF <condition> THEN [Statement(s)];
ELSIF <condition2> THEN [Statement(s)];
  ELSE [Statement(s)];
END IF;
```

This version should **only** be used to model sequential logic (we will see more in the next lecture)

Each of these sections should contain at least one, but can contain multiple statements

# Explicit Constructs

- Nested **IF ... END IF;** constructs can be replaced by the **CASE ... END CASE;** construct:

The `<case_variable>` can be a **SIGNAL, PORT, or a VARIABLE**

```
CASE <case_variable> IS
  WHEN <value1> => [Statement(s)];
  WHEN <value2> => [Statement(s)];
  WHEN <value3> => [Statement(s)];
  ...
  WHEN OTHERS => [Statement(s)];
END CASE;
```

Each of these sections should contain at least one, but can contain multiple statements

The **OTHERS** case covers for all situations not covered by the previous **WHEN** lines (similar **default:** in C++).

It is not required, but **highly recommended** to use!

- Note, the **CASE ... END CASE;** construct has no equivalent implicit form!

# Size Macros

- Assume following code

```
s_bitwise_and(0) <= s_input_vector(0) AND s_bit;
s_bitwise_and(1) <= s_input_vector(1) AND s_bit;
s_bitwise_and(2) <= s_input_vector(2) AND s_bit;
s_bitwise_and(3) <= s_input_vector(3) AND s_bit;
```

- We can simplify this code by using a macro

- ❖ For implicit process usage

```
Bitwise_and : FOR n IN 3 DOWNTO 0 GENERATE
  s_bitwise_and(n) <= s_input_vector(n) AND s_bit;
END GENERATE;
```

- ❖ For explicit process usage

```
FOR n IN 3 DOWNTO 0 LOOP
  s_bitwise_and(n) <= s_input_vector(n) AND s_bit;
END LOOP;
```

**Note:**  
These macros do **not** equal to a for loop as used in C++, they merely help us to compact our code

- Syntax

```
FOR <variable> IN <value1> DOWNTO <value2> LOOP
  [Statement(s)]
END LOOP;
```


```
<id> : FOR <variable> IN <value1> DOWNTO <value2> GENERATE
  [Statement(s)]
END GENERATE;
```

# Summary

□ We now have all the tools to create combinatorial logic:

- ❖ **SIGNAL's** → the wires of the system
- ❖ **Operators** → to model the functionality of the system
- ❖ **PROCESS'es** → which execute in parallel, and can be of two forms
  - Implicit: These processes are not contained in a **PROCESS** container and are in the form `<signal_name> <= <source>`
  - Explicit: These processes are in a **PROCESS** container, and the statements in these processes execute in program order
- ❖ **Statements** → help to express conditional logic (= multiplexing)
  - Implicit usage only: The **WHEN ... ELSE ...** construct
  - Explicit usage only: The **IF ... END IF;** and **CASE ... END CASE;** constructs
- ❖ **Size Macros** → helps to compact our code
  - Implicit usage: The **GENERATE** macro
  - Explicit usage: The **LOOP** macro

# Summary

 

All processes are defined in the body of the architecture

The order of the process (implicit and explicit) does not matter as they execute in **parallel**

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;

ENTITY full_adder IS
  PORT ( A      : IN  std_logic; -- A input
        B      : IN  std_logic; -- B input
        Cin    : IN  std_logic; -- Carry input
        SUM    : OUT std_logic; -- Sum output
        Cprop  : OUT std_logic; -- Carry propagate
        Cout   : OUT std_logic); -- Carry output
END full_adder;

ARCHITECTURE implementation_1 OF full_adder IS
  SIGNAL s_x8 : std_logic;
BEGIN
  SUM    <= A XOR B XOR Cin;
  Cout   <= s_x8;
  Cprop  <= s_x8 AND Cin;


  make_s8 : PROCESS( A , B , Cin )
  BEGIN
    s_x8 <= (A AND B) OR (Cin AND (A XOR B));
  END PROCESS make_s8;
END implementation_1;
```

We have **three** implicit processes

We have **one** explicit process
 
# Latches

```
latch : PROCESS ( clock , d )  
BEGIN  
    IF (clock = '1') THEN  
        q <= d;  
    END IF;  
END PROCESS latch;
```





- ❑ If **clock** equals **1**, **q** will be scheduled to be the value of **d**. At the end of the **PROCESS**, **q** will be assigned the value of **d**
- ❑ If **clock** equals **0**, **q** will **not** be scheduled any value because the **IF** statement is skipped. Therefore at the end of the **PROCESS**, **q** will **keep** its previous value!
- ❑ We described a **memory** element, namely a latch
  
# Latches

- ❑ Let's look at the simulation behavior

```
latch : PROCESS ( clock , d )  
BEGIN  
    IF (clock = '1') THEN  
        q <= d;  
    END IF;  
END PROCESS latch;
```




- ① **clock** triggers the **PROCESS** and **clock = 1** → **q** takes the value of **d**
- ① an event on **d** triggers the **PROCESS** and **clock = 1** → **q** takes the value of **d**
- ② an event on **clock** triggers the **PROCESS** and **clock = 0** → **q** **keeps** its previous value
- ③ an event on **d** triggers the **PROCESS** and **clock = 0** → **q** **keeps** its previous value

# Latches vs. Muxes

- Both latches and multiplexers are described through **IF** statements


```

 latch : PROCESS ( clock , d )
BEGIN
  IF (clock = '1') THEN
    q <= d;
  END IF;
END PROCESS latch;
    
```



```

 mux : PROCESS ( s , in0 , in1 )
BEGIN
  IF (s = '1') THEN
    out <= in1;
  ELSE
    out <= in0;
  END IF;
END PROCESS mux;
    
```




- The important difference is that in muxes there is **always a new value assigned** to signals or variables, whereas in latches sometimes nothing is assigned and they **keep their old value** (→ memory!)
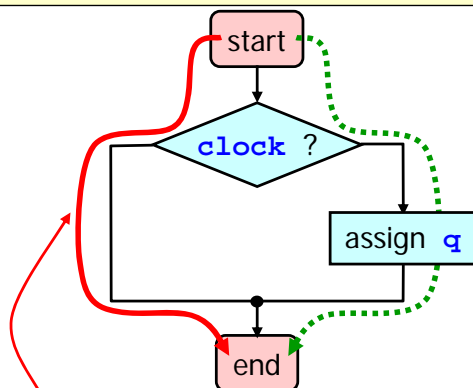
# Combinatorial or Sequential?

```

latch : PROCESS ( clock , d )
BEGIN
  IF (clock = '1') THEN
    q <= d;
  END IF;
END PROCESS latch;
    
```




At least one path between start and end of the process contains no assignment to **q**

→ **q** is the output of a sequential element

```

 mux : PROCESS ( s , in0 , in1 )
BEGIN
  IF (s = '1') THEN
    out <= in1;
  ELSE
    out <= in0;
  END IF;
END PROCESS mux;
    
```




All paths between start and end of the process contain at least one assignment to **out**


→ **out** is the output a combinatorial element
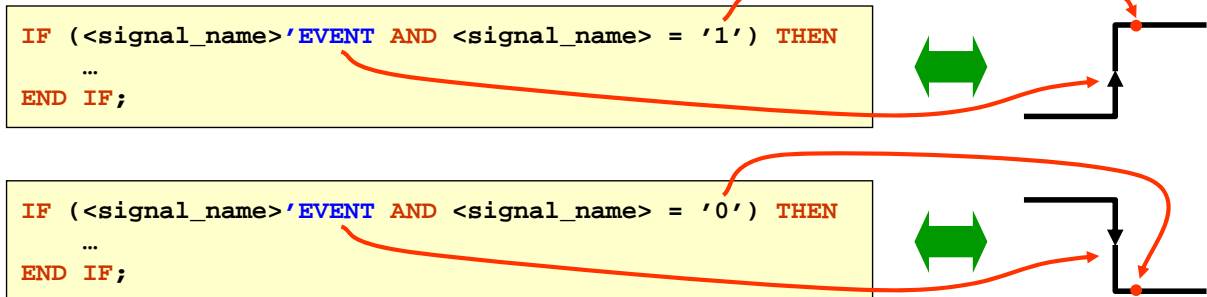
# Testing for Edges

- A signal with an **'EVENT'** modifier evaluates to true if there has been a high to low or low to high transition




 - An **EVENT** should **always** be used in combination with a test for the **current level**, because there exists **no hardware component** which is triggered by both transitions


 
# Flip-flops and Registers

```
flipflop : PROCESS ( clock , d )
BEGIN
  IF (clock'EVENT and clock = '1') THEN
    q <= d;
  END IF;
END PROCESS flipflop;
```





- If **there is a transition** and after it **clock** equals **1**, **q** will be scheduled to be the value of **d**, and at the end of the **PROCESS**, **q** will be assigned the value of **d**
- If there is no transition or **clock** equals **0**, **q** will **not** be scheduled any value because the **IF** statement is skipped. Therefore at the end of the **PROCESS**, **q** will **keep** its previous value!
- We also described a **memory** element, but this time it is a flip-flop
  
# Flip-flops and Registers

Let's look at the simulation behavior

```
flipflop : PROCESS ( clock , d )
BEGIN
  IF (clock'EVENT and clock = '1') THEN
    q <= d;
  END IF;
END PROCESS flipflop;
```




- ⓪ clock triggers the PROCESS and there is a raising edge → q takes the value of d
- Ⓛ an event on d triggers the PROCESS but there is no event on clock → q keeps its previous value
- Ⓜ an event on clock triggers the PROCESS but it is not a raising edge → q keeps its previous value
- Ⓝ an event on d triggers the PROCESS but there is no event on clock → q keeps its previous value
 
## A Bad Idea for a Flip-Flop

One could think of exploiting the sensitivity list...

```
flipflop : PROCESS ( clock , d )
BEGIN
  IF (clock'EVENT and clock = '1') THEN
    q <= d;
  END IF;
END PROCESS flipflop;
```




By the way, this is useless but not wrong...

This looks like a latch...

```
bad_flipflop : PROCESS ( clock )
BEGIN
  IF (clock = '1') THEN
    q <= d;
  END IF;
END PROCESS bad_flipflop;
```

**NO**

 

Simulators understand this...

...but most synthesizers ignore sensitivity lists and understand this!

...but it is only executed if clock changes!  
(normally a latch has d too here...)

# Reset


❑ A register does not have an initial state, and therefore needs a reset

❑ Two types of reset

**Note:** We will always use registers with a reset, either synchronous or asynchronous


❖ **Synchronous reset**
 
```
flipflop : PROCESS ( clock , reset , d )
BEGIN
  IF (clock'EVENT and clock = '1') THEN
    IF (reset = '1') THEN q <= '0';
      ELSE q <= d;
    END IF;
  END IF;
END PROCESS flipflop;
```



❖ **Asynchronous reset**
 
```
flipflop : PROCESS ( clock , reset , d )
BEGIN
  IF (reset = '1') THEN q <= '0';
  ELSIF (clock'EVENT and clock = '1') THEN
    q <= d;
  END IF;
END PROCESS flipflop;
```




# Registers, Signals, and Ordering

```
Delay_line : PROCESS ( clock , reset , d ,
                    s_q1 , s_q2 )
BEGIN
  IF (clock'EVENT AND clock = '1') THEN
    IF (reset = '1') THEN s_q1 <= '0';
      s_q2 <= '0';
      q3 <= '0';
    ELSE q3 <= s_q2;
      s_q2 <= s_q1;
      s_q1 <= d;
    END IF;
  END IF;
END PROCESS Delay_line;
```

```
Delay_line : PROCESS ( clock , reset , d ,
                    s_q1 , s_q2 )
BEGIN
  IF (clock'EVENT AND clock = '1') THEN
    IF (reset = '1') THEN s_q1 <= '0';
      s_q2 <= '0';
      q3 <= '0';
    ELSE s_q1 <= d;
      s_q2 <= s_q1;
      q3 <= s_q2;
    END IF;
  END IF;
END PROCESS Delay_line;
```

**YES!**

The two processes are identical

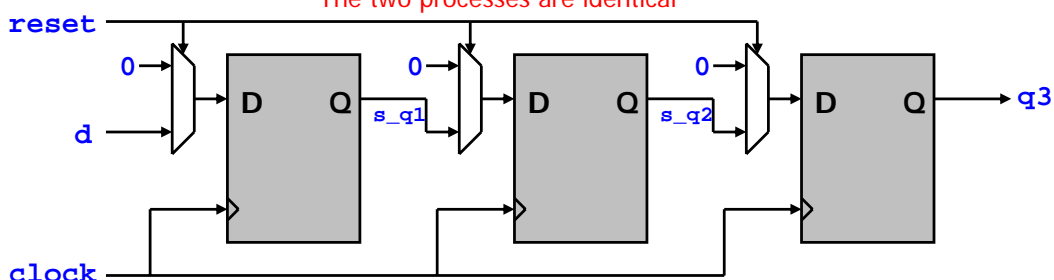



# Registers, Variables, and Ordering


```

Delay_line : PROCESS ( clock , reset , d ,
                    s_q1 )
    VARIABLE v_q2 : std_logic;
BEGIN
    IF (clock'EVENT AND clock = '1') THEN
        IF (reset = '1') THEN s_q1 <= '0';
            v_q2 := '0';
            q3 <= '0';
        ELSE q3 <= v_q2;
            v_q2 := s_q1;
            s_q1 <= d;
        END IF;
    END IF;
END PROCESS Delay_line;
    
```

```

Delay_line : PROCESS ( clock , reset , d ,
                    s_q1 )
    VARIABLE v_q2 : std_logic;
BEGIN
    IF (clock'EVENT AND clock = '1') THEN
        IF (reset = '1') THEN s_q1 <= '0';
            v_q2 := '0';
            q3 <= '0';
        ELSE s_q1 <= d;
            v_q2 := s_q1;
            q3 <= v_q2;
        END IF;
    END IF;
END PROCESS Delay_line;
    
```

 NO!  
The two processes are **different!**



## Components

- ❑ We can introduce a hierarchy by using **COMPONENT**'s
- ❑ A **COMPONENT** is a reference to an **ENTITY**
- ❑ The syntax of a **COMPONENT** is

```

COMPONENT <entity_name>
    PORT ( ... );
END COMPONENT;
    
```

Each **COMPONENT** requires a reference to the corresponding **ENTITY**

Each **COMPONENT** has the same port section as it's corresponding **ENTITY**

- ❑ The **COMPONENT** is defined in the declaration section of an **ARCHITECTURE**

# Usage of Components

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;

ENTITY full_adder IS
  PORT ( A      : IN  std_logic; -- A input
        B      : IN  std_logic; -- B input
        Cin    : IN  std_logic; -- Carry input
        SUM    : OUT std_logic; -- Sum output
        Cout   : OUT std_logic); -- Carry output
END full_adder;

ARCHITECTURE implementation OF full_adder IS
BEGIN

  SUM <= A XOR B XOR Cin;
  Cout <= (A AND B) OR (Cin AND (A XOR B));

END implementation;
```

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;

ENTITY adder IS
  PORT ( A      : IN  std_logic_vector( 3 DOWNTO 0);
        B      : IN  std_logic_vector( 3 DOWNTO 0);
        Cin    : IN  std_logic;
        SUM    : OUT std_logic_vector( 3 DOWNTO 0);
        Cout   : OUT std_logic);
END adder;

ARCHITECTURE implementation OF adder IS
  COMPONENT full_adder
  PORT ( A      : IN  std_logic; -- A input
        B      : IN  std_logic; -- B input
        Cin    : IN  std_logic; -- Carry input
        SUM    : OUT std_logic; -- Sum output
        Cout   : OUT std_logic); -- Carry output
  END COMPONENT;

  SIGNAL s_carries : std_logic_vector( 4 DOWNTO 0);
BEGIN
  s_carries(0) <= Cin;
  fas : FOR n IN 3 DOWNTO 0 GENERATE
    fa : full_adder
      PORT MAP ( A  => A(n),
                B  => B(n),
                Cin => s_carries(n),
                SUM => SUM(n),
                Cout => s_carries(n+1) );
  END GENERATE fas;
END implementation;
```

The reference to the **ENTITY full\_adder** with the same **PORT** section

Each **COMPONENT** needs a unique identifier

And here we connect the **PORT**'s of the component with the **SIGNAL**'s to form the new functionality

## Summary Signals, Variables, and Parallelism

- ❑ For a **SIGNAL**, the **<=** has a different meaning in an implicit **PROCESS**, and when used in a statement (explicit **PROCESS**)
  - ❖ Using **<=** in an implicit **PROCESS** means **assign immediately**
  - ❖ Using **<=** in an explicit **PROCESS** means **schedule an assignment**
- ❑ A **VARIABLE** can **only** exist in an explicit **PROCESS**, and is assigned a value by using **:=**, where
  - ❖ Using **:=** means **assign immediately**
- ❑ Implicit and explicit **PROCESS**'es are defined inside the **body** of the **ARCHITECTURE**, and execute **in parallel**
- ❑ Statements are defined inside the **body** of an explicit **PROCESS**, and execute **in program order**


# Summary

## Sequential Components

- ❑ Sequential elements can only be made by using an explicit **PROCESS**
- ❑ Memory elements can only be introduced in case the **PROCESS** contains a non-assigned path, otherwise a multiplexer is described
- ❑ There are two kinds of memory elements:

- ❖ Latches:
 
```
latch : PROCESS ( clock , d )  
BEGIN  
    IF (clock = '1') THEN  
        q <= d;  
    END IF;  
END PROCESS latch;
```



- ❖ Flip-flops:

```
flipflop : PROCESS ( clock , d )  
BEGIN  
    IF (clock'EVENT and clock = '1') THEN  
        q <= d;  
    END IF;  
END PROCESS flipflop;
```

